
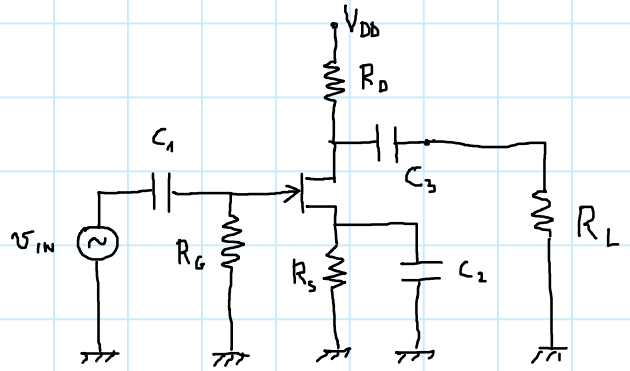


METODO ANALITICO

JFET 12

PER IL CIRCUITO STATICO

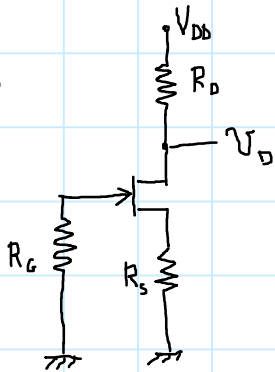

POSSO SCRIVERE: $I_D = I_{DSS} \left[1 - \frac{V_{GS}}{V_{GS OFF}} \right]^2$


$V_{GS} = -R_S I_D$

$I_D = I_{DSS} \left[1 + \frac{R_S I_D}{V_{GS OFF}} \right]^2$

$$I_D = I_{DSS} \left[1 + 2 \frac{R_S I_D}{V_{GS OFF}} + \frac{R_S^2 I_D^2}{V_{GS OFF}^2} \right]$$

$$\frac{R_S^2 I_{DSS} I_D^2}{V_{GS OFF}^2} + \left(\frac{2 R_S I_{DSS}}{V_{GS OFF}} - 1 \right) I_D + I_{DSS} = 0$$

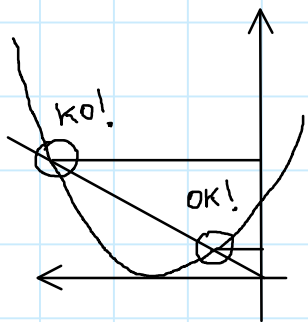Ricavo solo 1 sol. $\therefore I_{D1} = \frac{-b - \sqrt{\Delta}}{2a}$



Nota I_D ricavo V_D :
 $V_D^S = V_{DD} - V_S = V_{DD} - R_S I_D$


PER IL CIRCUITO DINAMICO:

GUADAGNO DI TENSIONE
 $A_V = \frac{V_{DS}}{V_{GS}}$

$$g_{fs} = \frac{\Delta I_D}{\Delta V_{GS}} \Rightarrow g_{fs} = \frac{i_D}{V_{GS}} \rightarrow \begin{cases} V_{GS} = \frac{i_D}{g_{fs}} \\ V_D = -R_D i_D \end{cases}$$

REGIME STATICO REGIME DINAMICO

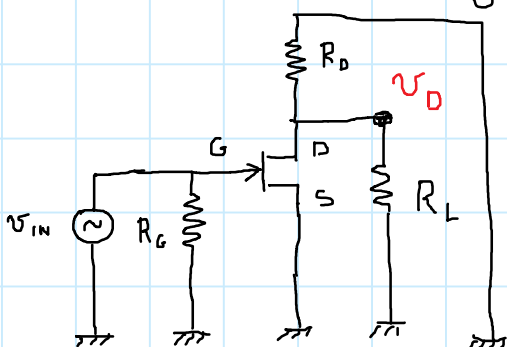Quindi $A_V = \frac{-R_D i_D}{i_D / g_{fs}} = -R_D \cdot g_{fs} (*)$



$V_{GS} = v_{IN}$

$v_D^d = v_{DS} = A_V \cdot v_{GS} = -R_D g_{fs} v_{IN}$

$v_D = V_D^s + v_D^d$

IN ASSENZA DI R_L

CON CARICO.

JFET 13

Applicazione del metodo analitico al circuito già esaminato

$$\begin{cases} I_D = I_{DSS} \left[1 - \frac{V_{GS}}{V_{GS(OFF)}} \right]^2 & \text{Parabola} \\ I_D = -\frac{1}{R_S} V_{GS} & \text{Retta} \end{cases}$$


$$\frac{R_S^2 I_{DSS}}{V_{GS(OFF)}^2} I_D^2 + \left(\frac{2R_S I_{DSS}}{V_{GS(OFF)}} - 1 \right) I_D + \frac{I_{DSS}}{c} = 0$$

$R_S = 1,00E+3$
$V_{GS(OFF)} = -3$
$I_{DSS} = 12,00E-3$

$a = 1,33E+3$
$b = -9$
$c = 12,00E-3$

$I_{D1} = 4,92E-3$
$I_{D2} = 1,83E-3$

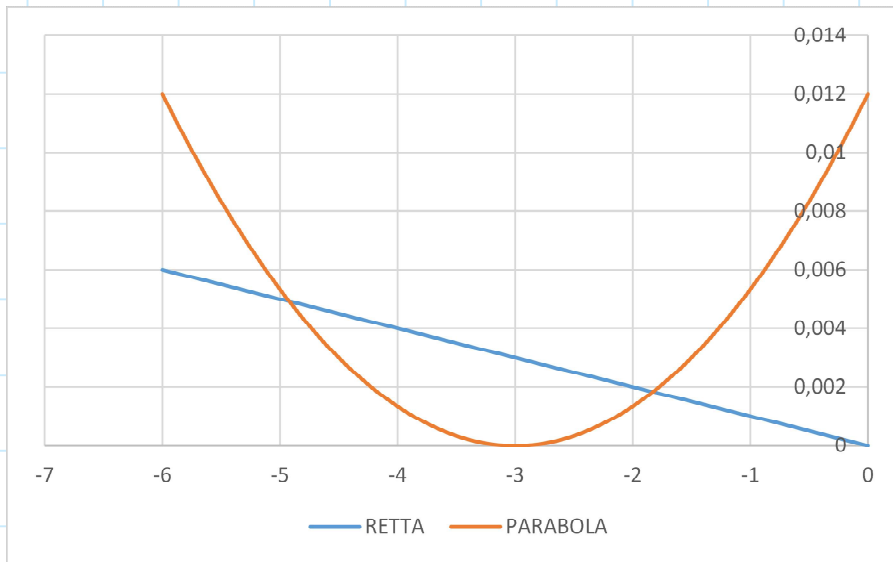$V_{GSQ} = -R_S I_{D2} = -1,83$
$V_{D(\text{statico})} = V_{DD} - R_D I_{D2} = 7,98$



Per il JFET 2N3819 $g_{fs0} = 5,5 \text{ mS}$ DATA SHEET $\rightarrow 7,8$ SIMULAZIONE

$$g_{fs} = g_{fs0} \left[1 - \frac{V_{GS}}{V_{GS(OFF)}} \right] = 5,5 \text{ m} \left[1 - \frac{-1,83}{-3} \right] = 2,145 \text{ mS}$$

$$v_D^d = -\frac{R_D R_L}{R_D + R_L} g_{fs} v_{in} = -\frac{2,2 \cdot 10^4}{12,2} \cdot 2,145 \text{ m} \cdot v_i \approx -3,87 \cdot v_{in}$$

$$v_D = V_D^s + v_D^d = 7,89 - 5,5 \cdot 100 \text{ m} \sin(\omega t) = 7,89 - 0,5 \sin(\omega t)$$